


Pre-Lab:

Q1: Yes, Batteries, and Amplifiers with OP-AMPS can both have voltages without a current.

When input voltages are the same,

output at 0V is occurs.

Also, current decreases along conductors

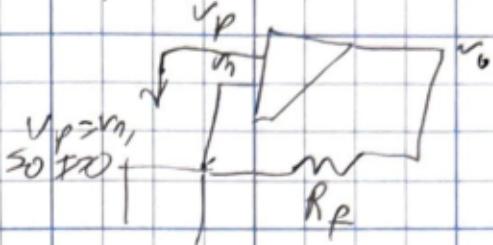

Q2: Yes, current through conducting wire has little to no voltage drop.

Q3: Typically 30 to 50 mV. Not a lot.

Q4: Feedback into one of the input terminals


Q5: $V_p = V_n$, the two input terminals have equal voltage

Q6: An voltage amplifier, limits at a peak ±15V.


If the AV between terminals is too large, reach the op-amp voltage peak.
 = comparator

7. $V_o = A_v(V_p - V_n)$ - difference in voltage times gain A_v .

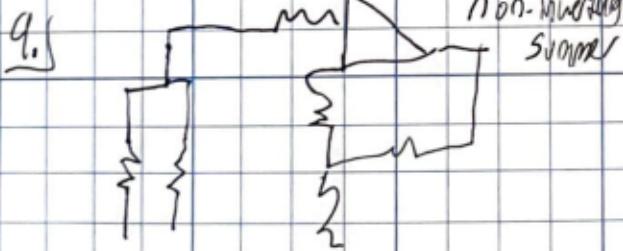8. It can be, as long as the difference in voltage between the two is small.




non-inverting

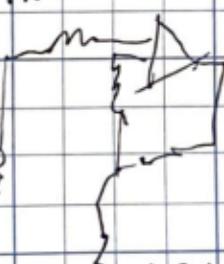

Both inverting & non-inverting summers attenuate the input voltage

10. Linearity. $T(x_1) = T(x_1) + T(x_2) = T(x_1 + x_2)$

11. a.)

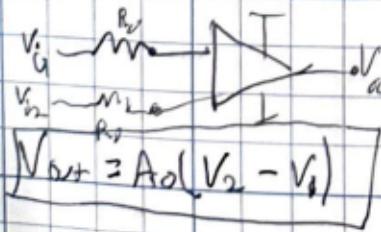

b.) $V_p = V_n$

$V_o = \frac{-V_1}{R_F} R_S$

$$\frac{V_o}{V_1} = \frac{-R_F}{R_S}$$


$$= -\frac{R_2}{R_1}$$

$$I_{V_1} = -IR, \approx IR_F$$

$$V_o = IR_F$$

1) Comparators	Measured						Expect
	V_1	V_2	$V_{0(\text{th})}$	V_1	V_2	V_o	
	5.00	4.7					
	4.20	1.1					
	4.05	2.05					
	3.85						
	3.80						
+ve input	$V_{1, \text{in}}$	$V_{2, \text{in}}$					
	3.00						


2) Inv. AMP.

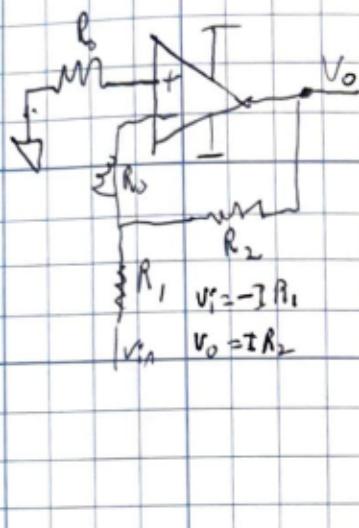

Th.	Measured				Expect
	$V_{1, \text{in}}$	$V_{0(\text{th})}$	V_{in}	V_{out}	
2.00V					
1.50V					
7					
5					
7.5					
5					
-7.5					
-7					
-5					
-7.5					
-2.0					

$$\frac{V_o}{R_2} = -\frac{V_1}{R_1}, \quad \frac{V_o}{V_1} = -\frac{R_2}{R_1}$$



3) Instrumental Amp

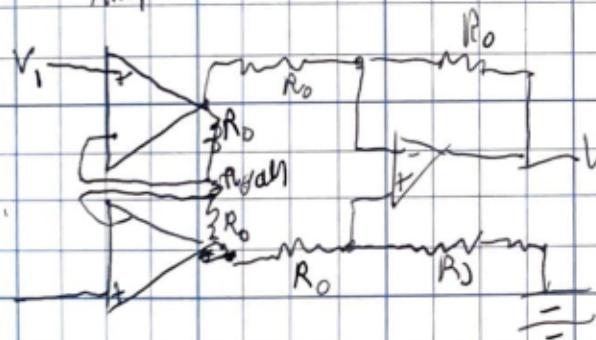

target	expect	Measured			
		$\Delta V_{1, \text{in}}$	ΔV_2	V_1	V_2
100mV	50mV				
50mV	20				
20	10				
10	1				
1	-1				

Q3 | SW 10db, -M11ce plots
 2 Dots w/ 11

1) Comparator

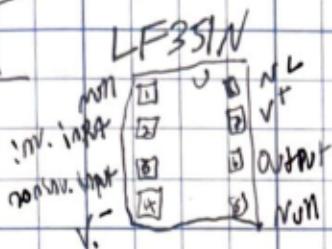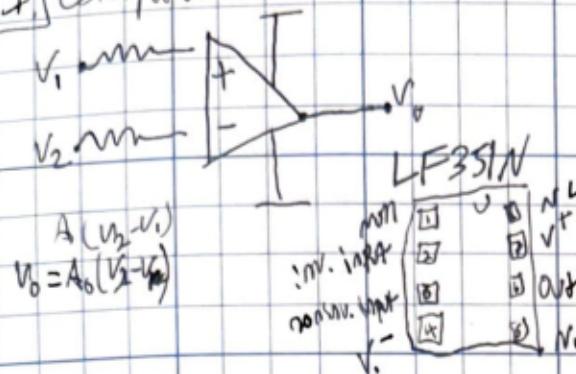

I Data collection went well, Data symmetric.


Looks like OP-Amp. max is 8.5 V.

V_0 Flips sign when $V_2 > V_1$, equal voltages.

Next day will do 2#3


Measured					
V_1 (Th.)	V_2 (Th.)	V_0 (Th.)	V_1	V_2	V_0
5.00	4.00	-1.63	5.00	4.00	-1.63
4.20	11	"	4.20	"	-7.57
4.05			4.05		-7.50
3.95			3.95		-8.51
3.85			3.85		-8.50
3.80			3.80		-8.50
3.00	11		2.99		8.49
5.00	-4.00		-5.00	-4.00	8.50
-4.20			-4.20	11	8.50
-4.05			-4.06		8.50
-3.95			-3.95		-7.51
-3.85			-3.85		-7.56
-3.80	11		-3.80		-7.57
-2.00			-3.00		-7.63

2) Inverting Amplifiers

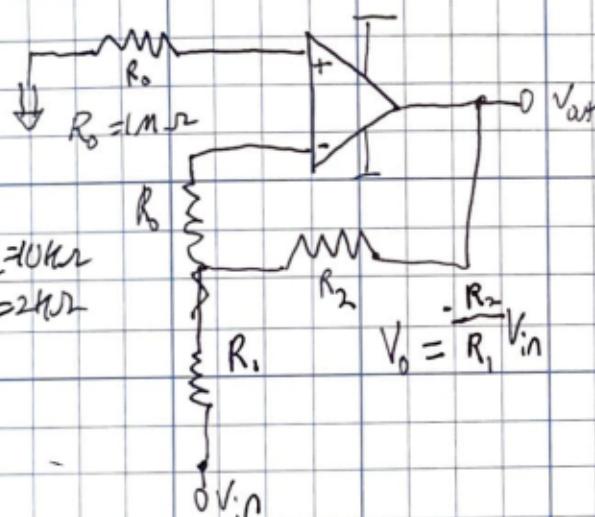


Theory				Measured	
V_{in} (Th.)	V_{out} (Th.)	V_m	V_{out}		
2.00	1.970	-2.37			
1.50	1.532	-2.29			
0.7	0.739	-3.62			
0.5	0.514	-2.51			
0.1	0.1035	-0.50			
-0.1	-0.1022	0.49			
-0.5	-0.508	2.48			
-0.7	-0.693	3.34			
-1.50	-1.502	7.35			
-2.00	-2.001	8.11			

δR_2
 $\sqrt{2} \gamma / 23$

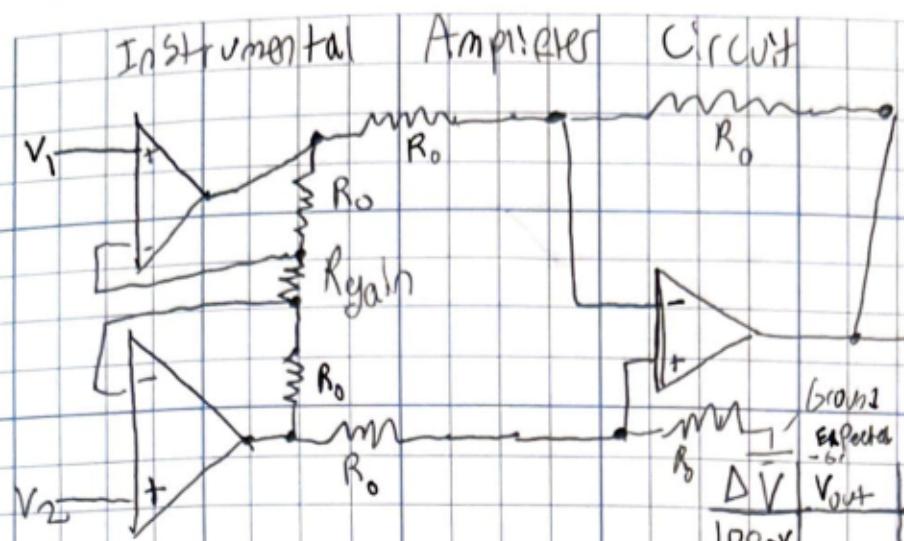

$$\text{gain } A = \frac{V_{\text{out}}}{\Delta V} = \left(1 + \frac{2R_o}{R_{\text{gains}}}\right)$$

more LF351N

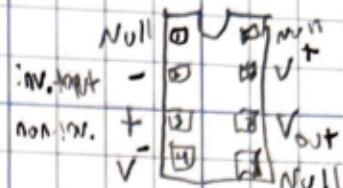

$$R_o = 1 \text{ M}\Omega$$


$$R_g = 20 \text{ k}\Omega$$

ΔV

ΔV	V_{out}	V_1	V_2	$V_2 - V_1$	V_{out}
100mV	4.172	4.272		-0.100	8.50
50	4.226	4.272		-0.046	8.50
20	4.260	4.272		-0.012	6.14
10	4.268	4.272		-0.004	5.42
1	4.276	4.272		-0.004	3.96
-1	4.282	4.272		0.010	3.00
-15	4.290	4.272		0.018	0.9
-20	4.290	4.272		0.018	0.43
-50	4.327	4.272		0.055	-3.91
-100mV	4.375	4.272		0.103	-7.57

will

Day 3: Linear integrator

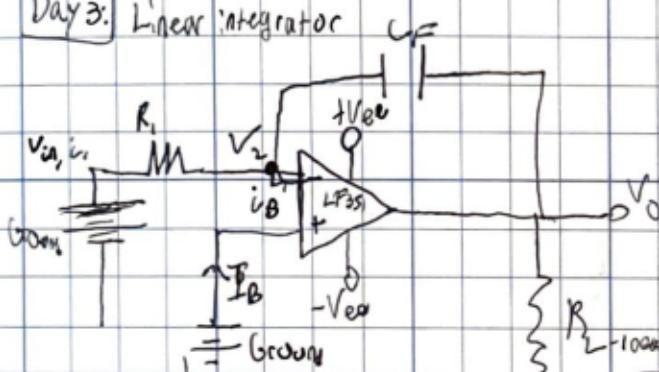

$$V_0 = -\frac{1}{R_1 C f} \int v_{\text{in}} dt$$

$$R = R_2 + 10 \text{ k}\Omega / 2, C_f = 100 \text{ nF}$$

$$R_1 = R_2 = 10 \text{ k}\Omega, C_f = 100 \text{ pF}$$

will


$\sum R = 100 \text{ k}\Omega$ INPUT OUTPUT 14.6/2

Ground 15 kHz, 90 mV Triangle, 24.0 mV, Same Freq
 Sine 21 kHz, 130 mV Triangle, 16.6/2 V, Same Freq
 Sine 21 kHz, 130 mV Cosine, 11.4/2, Same Freq
 Sine 71 kHz, 130 mV Cosine, 4.60/2, Same Freq
 Cosine 41 kHz, 130 mV Cosine, 4.60/2, Same Freq
 Triangle 41 kHz, 130 mV Sine, 5.20/2, Same Freq

Overall, good Results. Plots and images of circuits will be attached to the PDF. No plot for integrator, just pulse behavior to integral output.
 Frequency matches shape matches integral.


Phys382 Lab Notes - Op Amp - Maxwell Rizzo

1. Comparator

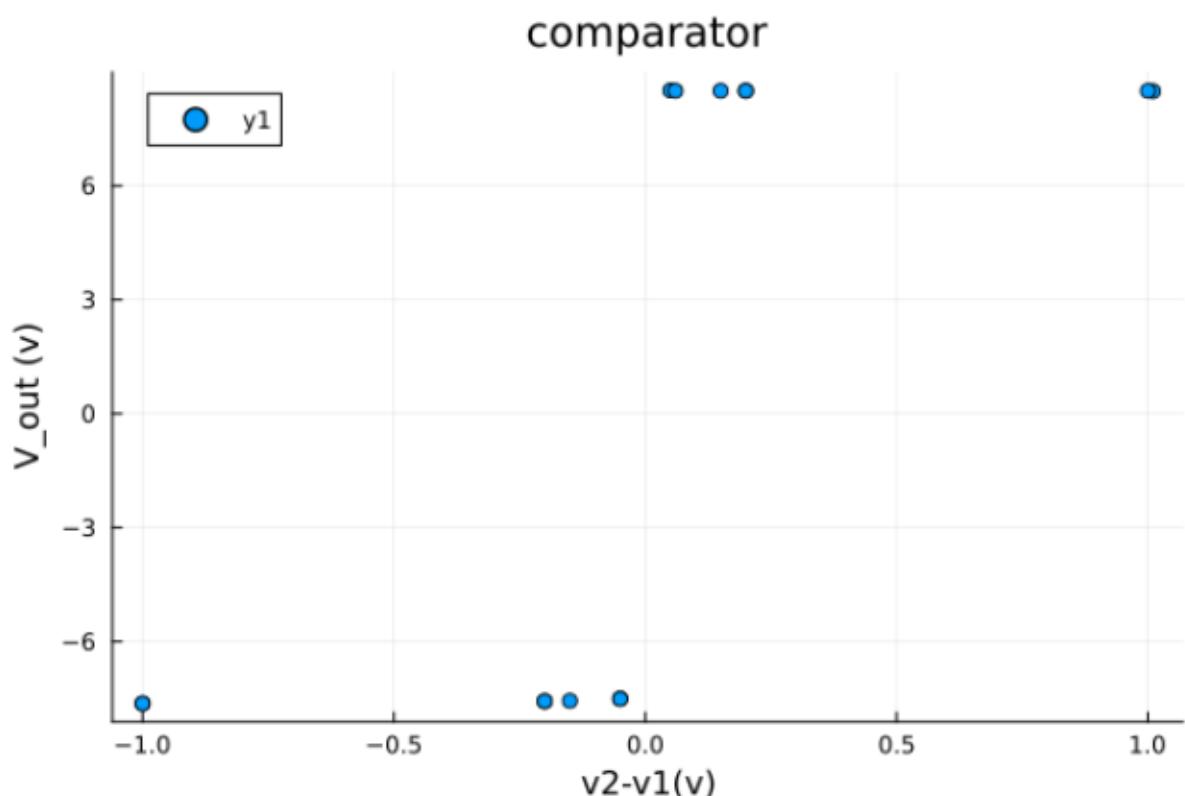


Op-Amp rails out instantly, step function. Expected result.

2. Inverting Amp

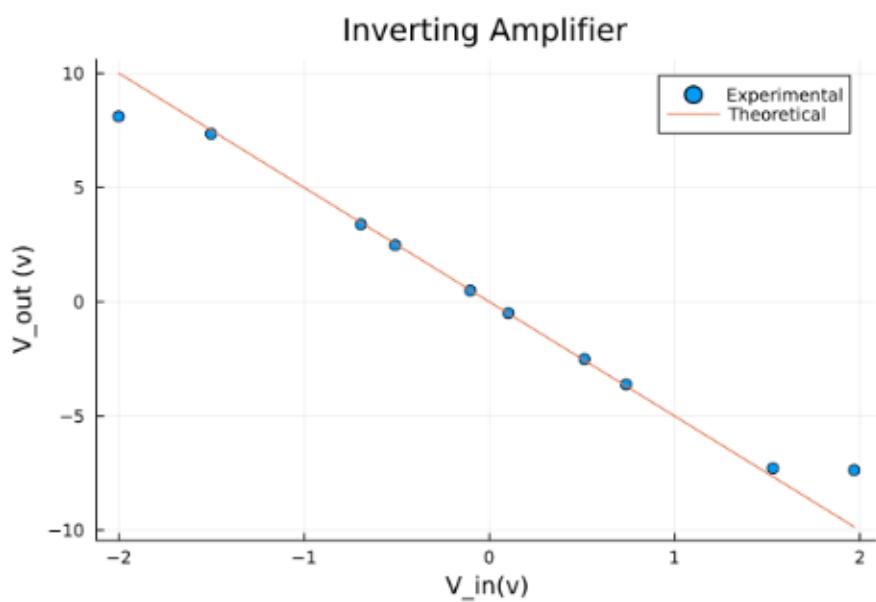


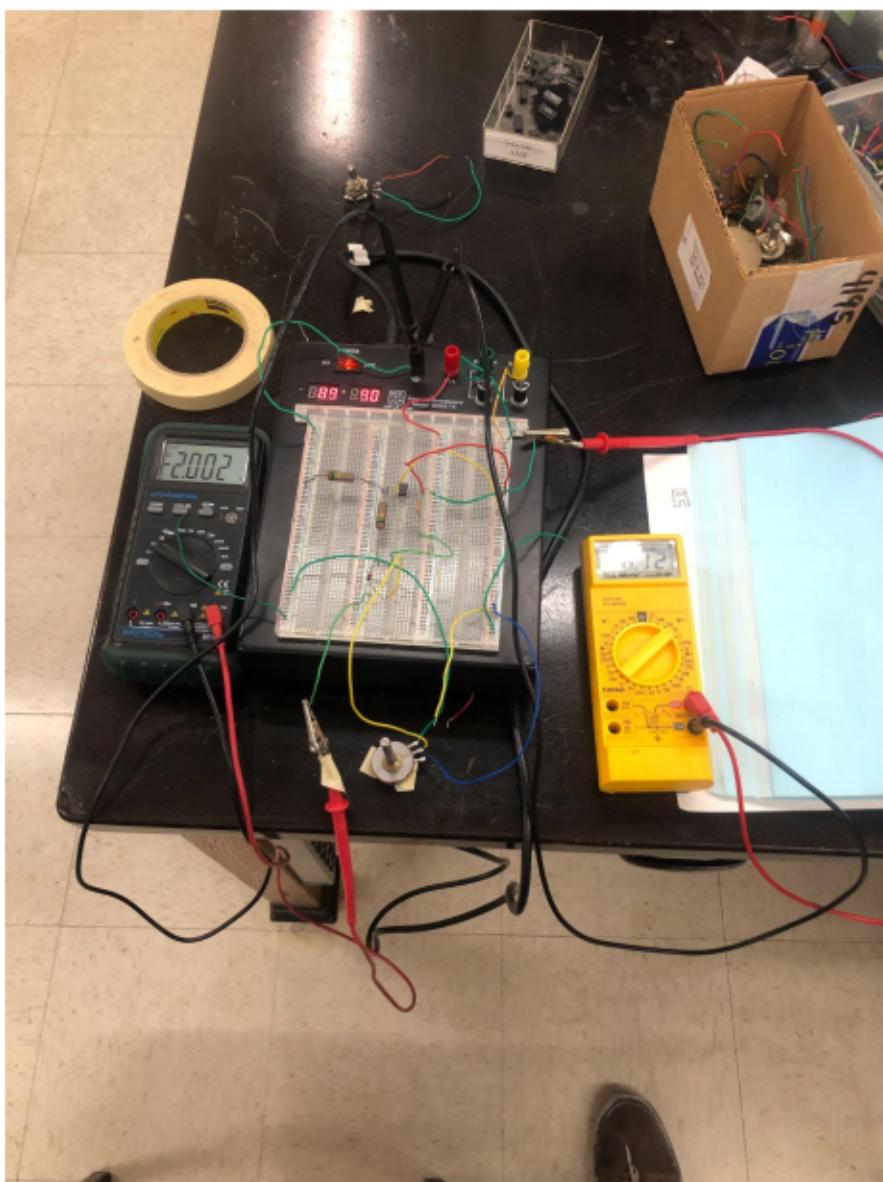Data matches the theoretical model very closely, good data.



Inverting Amplifier Circuit setup


3. Instrumental Amplifier

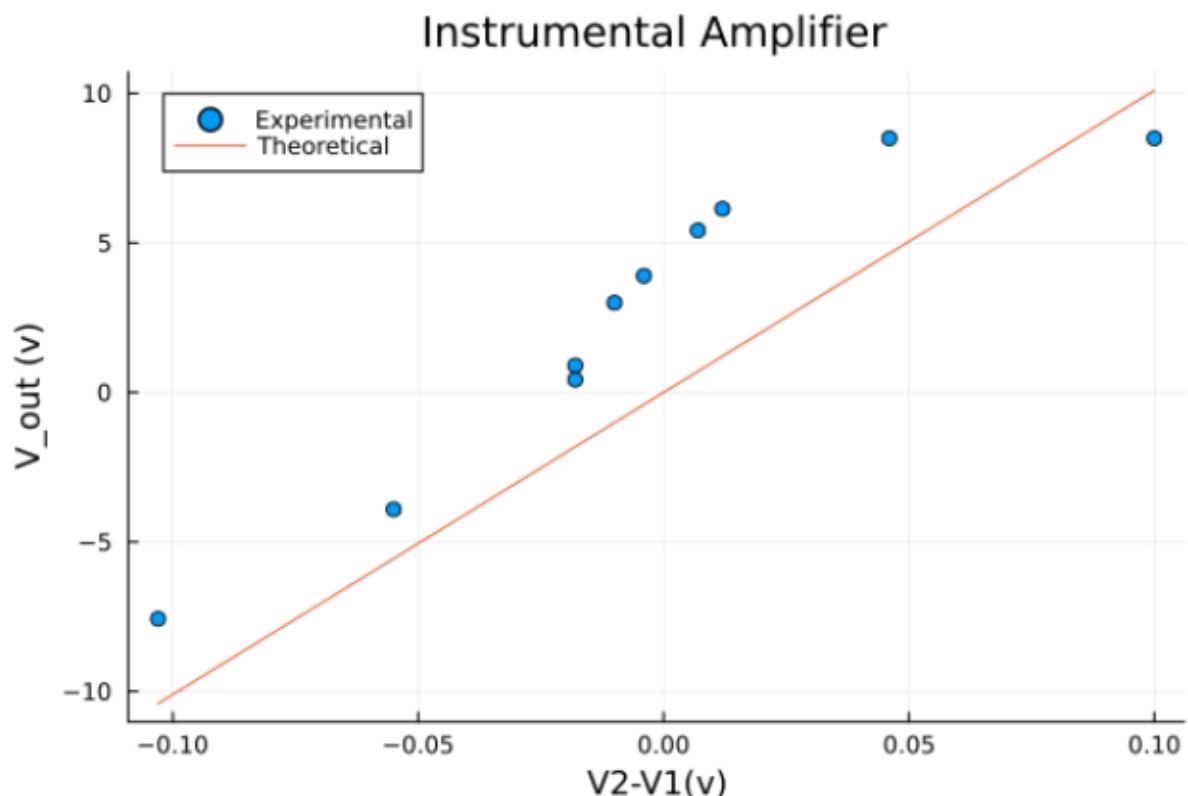

Experimental data matches theoretical model closely again, good data. Apparatus photo on next page.

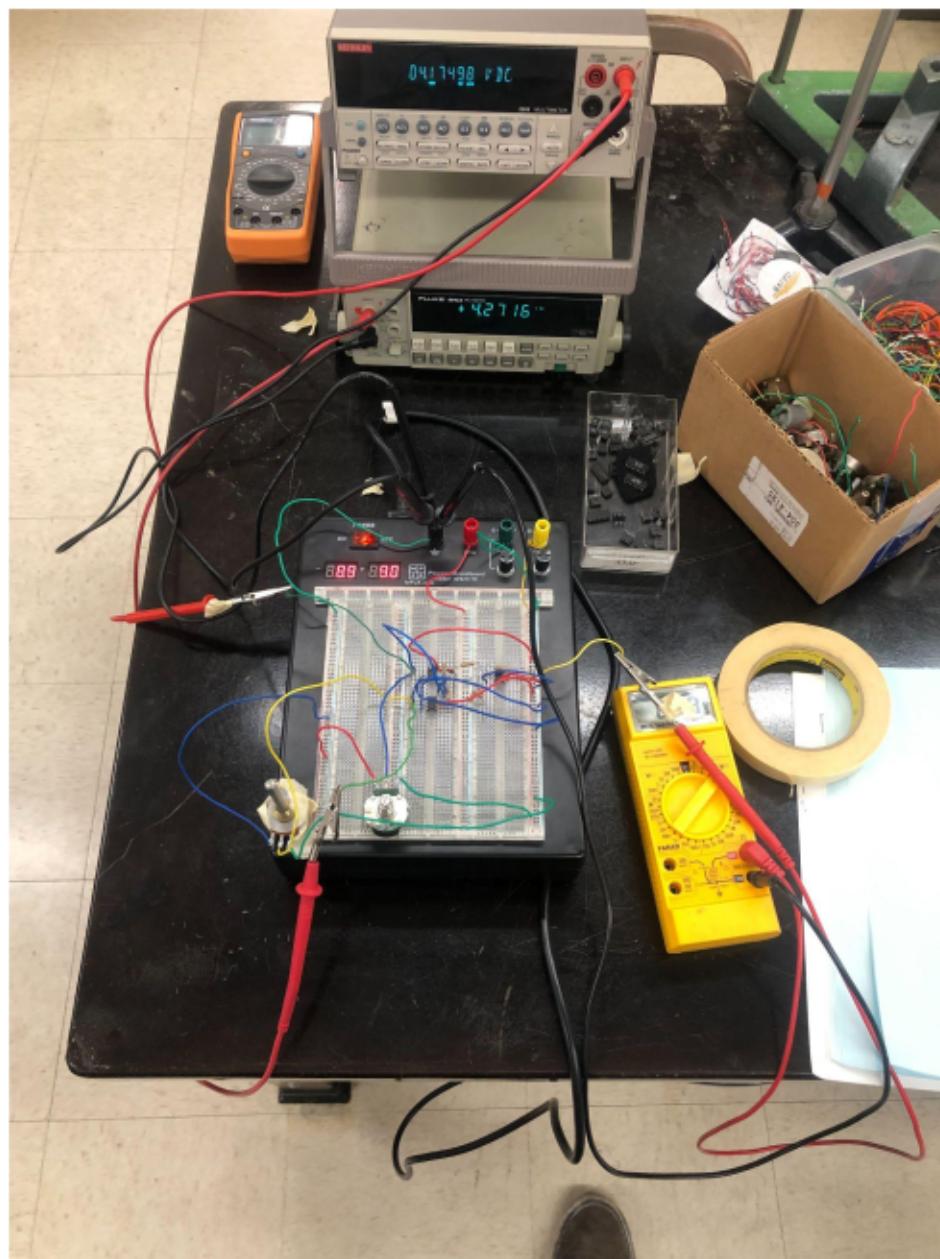4. Linear Integrator

No plot made, qualitative behavior and response recorded and detailed in lab notebook.



Apparatus for Instrumental amplifier